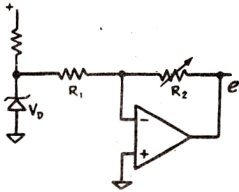
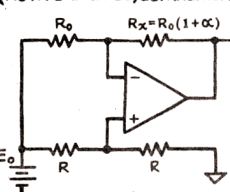
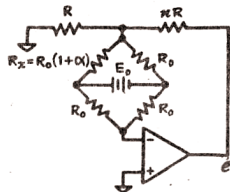
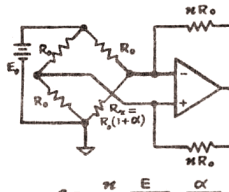

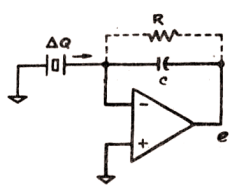
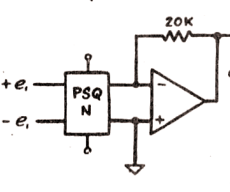
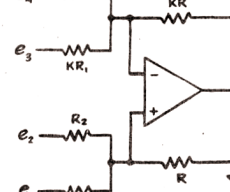
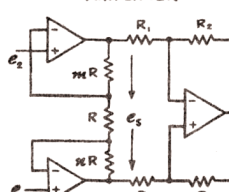
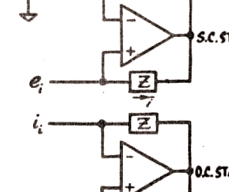
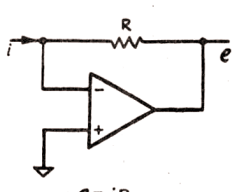
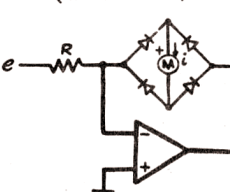
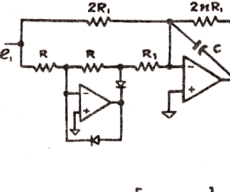
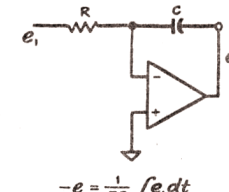
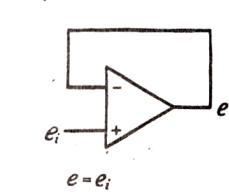
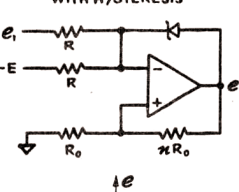
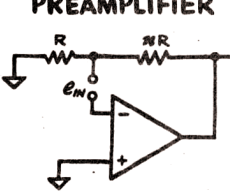
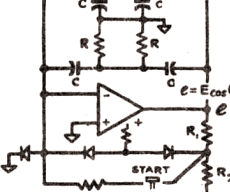
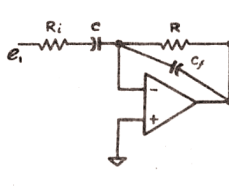
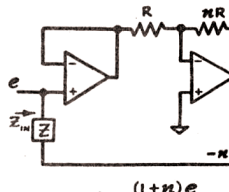
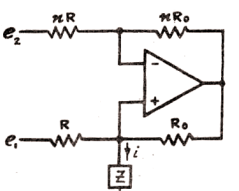
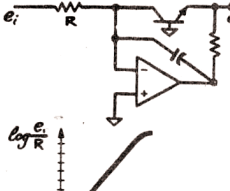
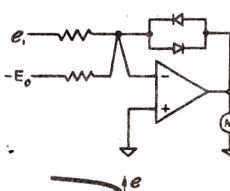
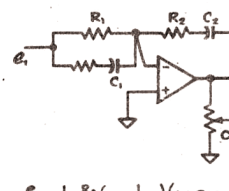
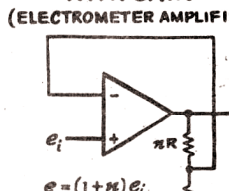


TYPICAL OPERATIONAL AMPLIFIER APPLICATIONS
for MODELLING, MEASURING, MANIPULATING, and MUCH ELSE

<p>PRECISION VARIABLE VOLTAGE SOURCE</p>  <p>$e = -V_D \frac{R_2}{R_1}$</p>	<p>BRIDGE AMPLIFIER (ACTIVE BRIDGE, ULTRALINEAR)</p>  <p>$e = -\frac{1}{2} \alpha E_0$</p>	<p>BRIDGE AMPLIFIER (FLOATING SUPPLY)</p>  <p>$e = (1+n) \alpha \frac{E_0}{4} \left[\frac{1}{1+\frac{n}{2}} \right] \approx (1+n) \alpha \frac{E_0}{4}$</p>	<p>BRIDGE AMPLIFIER (ONE END GROUNDING)</p>  <p>$e = -\frac{n}{2} \frac{E_0}{1+\frac{n}{2}} \frac{\alpha}{1+\alpha}$ $\frac{n}{2} = \frac{n}{2} \frac{E_0}{E_0} \frac{\alpha}{1+\alpha}$</p>	<p>BRIDGE AMPLIFIER (MID-POINT GROUNDING)</p>  <p>$e = \frac{E_0}{4} n \alpha \left[\frac{1}{1+\frac{n}{2}} \right] \approx \frac{E_0}{4} n \alpha$</p>
<p>CHARGE AMPLIFIER</p>  <p>$-e = \frac{\Delta Q}{C}$</p>	<p>PRECISE WIDE BAND SQUARER</p>  <p>$e = \frac{1}{10} e_i^2$</p>	<p>ADDING SUBTRACTOR</p>  <p>$e = \frac{R}{R_1} e_1 + \frac{R}{R_2} e_2 - \frac{R}{R_3} e_3 - \frac{R}{R_4} e_4$</p>	<p>LOW-COST, LOW-NOISE HIGH-INPUT IMPEDANCE DIFFERENTIAL-TO-SINGLE-ENDED AMPLIFIER</p>  <p>$e_s = (1+m+n)(e_1 - e_2)$ $e = \frac{R_1}{R_2} e_s$</p>	<p>NEGATIVE IMPEDANCES</p>  <p>S.C. STABLE D.C. STABLE $Z_N = \frac{R}{1+n} = -\frac{Z}{n}$</p>
<p>CURRENT-TO-VOLTAGE TRANSRESISTOR</p>  <p>$-e = iR$</p>	<p>PRECISION AC-DC CONVERTER (METER OUTPUT)</p>  <p>$i = \left \frac{e_i}{R} \right$</p>	<p>PRECISION FULL-WAVE RECTIFIER-FILTER "AC-DC CONVERTER"</p>  <p>$e = n e_i \left[\frac{1}{1+2R_2 C P} \right]$</p>	<p>STABLE INTEGRATOR</p>  <p>$-e = \frac{1}{RC} \int e_i dt$</p>	<p>FOLLOWER (ELECTROMETER)</p>  <p>$e = e_i$</p>
<p>PRECISE VOLTAGE OR CURRENT COMPARATOR WITH HYSTERESIS</p>  <p>$e = E$</p>	<p>FLOATING SOURCE PREAMPLIFIER</p>  <p>$e = (1+n) e_{IN}$</p>	<p>PRECISION OSCILLATOR</p>  <p>$\omega_0 = \frac{1}{RC}$ $E \approx \frac{RC}{R_2} E_0$</p>	<p>STABLE LOW-NOISE DIFFERENTIATOR</p>  <p>$-\frac{e}{e_i} = [RCp] \left(\frac{1}{(1+RCp)(1+R_1 C_1 p)} \right)$</p>	<p>IMPEDANCE SCALER</p>  <p>$i_{IN} = \frac{(1+n)e}{Z}$ $Z_{IN} = \frac{Z}{1+n}$</p>
<p>VARIABLE CONTROLLED CURRENT SOURCE</p>  <p>$i = \frac{e_1 - e_2}{R}$</p>	<p>PRECISE WIDE-RANGE LOGARITHM 9-DECADES</p>  <p>$\log \frac{e_i}{R}$</p>	<p>GRADED NULL MEASUREMENT</p>  <p>$e = E_0$</p>	<p>CONTROLLER (3-TERM)</p>  <p>$-\frac{e}{e_i} = \frac{1}{\alpha} \frac{R_2}{R_1} \left(1 + \frac{1}{R_1 C_1 p} \right) (1 + R_1 C_1 p)$ PROPORTIONAL INTEGRAL DERIVATIVE</p>	<p>FOLLOWER WITH GAIN (ELECTROMETER AMPLIFIER)</p>  <p>$e = (1+n) e_i$</p>

For information on any of the circuits shown here consult PHILBRICK or their representative nearest to you.